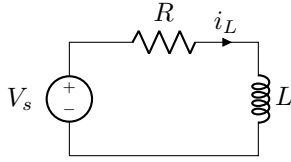


# Lecture 27, Mar 21, 2022

## Step Response of an RL Circuit

- Consider an RL circuit with an voltage source that turns on at  $t = 0$ , with the inductor initially charged with a current of  $I_0$ :



- KVL: 
$$-V_s + Ri_L(t) + L\frac{di_L}{dt} = 0$$

$$\Rightarrow i_L(t) - \frac{V_s}{R} = -\frac{L}{R} \frac{di_L}{dt}$$

$$\Rightarrow \int \frac{1}{i_L(t) - \frac{V_s}{R}} di_L = \int -\frac{1}{L/R} dt$$

$$\Rightarrow \ln\left(i_L(t) - \frac{V_s}{R}\right) + K = -\frac{t}{L/R}$$

$$\Rightarrow i_L(t) = \frac{V_s}{R} + Ae^{-\frac{t}{L/R}}$$

\* Using the initial condition of  $i_L(0) = I_0 \Rightarrow A = I_0 - \frac{V_s}{R}$

\*  $i_L(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R}\right)e^{-\frac{t}{L/R}} = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R}\right)e^{-\frac{t}{\tau}}$

\*  $v_L(t) = L\frac{di_L}{dt} = (V_s - RI_0)e^{-\frac{t}{L/R}}$

- The current starts at  $I_0$  and exponentially decays towards  $\frac{V_s}{R}$ , the final value for current (at which point the inductor is a short circuit)
  - At  $t = 0$  this is accompanied by a jump in the voltage
- The time constant  $\tau$  is given by  $\frac{L}{R}$
- As with the RC case,  $i_L(t) = i_L(\infty) + (i_L(0) - i_L(\infty))e^{-\frac{t}{\tau}}$ 
  - $i_L(\infty) = \frac{V_s}{R}$  because the inductor becomes a short circuit
  - $i_L(0) = I_0$